

Design of Sequential Logic: Flip flops, counter, state machine, stacks

1 Today's goal

- Learn how to use always and if statements to design flip flops.
- Learn how to design sequential logic such as counters, state machines and stacks.
- Learn how to write the postfix notation of a formula.

2 Today's contents

Step 1 Write a flip flop(List 1) and its test bench(List 2), and perform the simulation to confirm that it works properly.

Step 2 *Check 1* Write a counter(List 3) and its test bench (List 4) and perform the simulation to confirm that it works properly.

Step 3 *Check 2* Write a top module (List 5) of the counter and its ucf (List 6). Implement the bit file in the FPGA and confirm that it works correctly.

Step 3 *Check 3* Write a state machine (List 7) and its test bench (List 8). Perform the simulation.

Step 4 *Check 4* Write a top module (List 9) and implement the state machine using ucf (List 10) in the FPGA.

Step 5 *Check 5* Write a stack (List 11), an operation stack (List 12) and its test bench (List 13). Perform the simulation.

3 Flip flops

In sequential logic, the output depends on the past and the present input. To implement sequential logic, flip flops (D-flip flops) are used to store the information of the past input. Table 1 shows the behavior of the flip flop. It has 3 input bits, *d* (data input), *clk* (clock), and *reset*, and one output bit, *q* (data output).

Table 1: Behavior of a Flip flop

Input		Output
clk	reset	q
-	0	0 (Asynchronous reset)
↑	1	d (Synchronous latch)
not ↑	1	previous q(keeps the same value)

In the event list in List 1, “posedge *clk*” and “negedge *reset*” mean rising edge of *clk* and falling edge of *reset*, respectively. Thus, if event *negedge reset* occurs, *reset* is always 0, and *q <= 0* is executed. In the event of *posedge clk*, we have two cases:

- if *reset* is 0, then *q <= 0* is executed, although *q* is 0 before the event.
- if *reset* is 1, then *q <= d* is executed.

Thus, the flip flop in List 1 satisfies the specification in List 1.

List 1: Flip flop ff.v

```
1 module ff(clk, reset, d, q);
2
3   input clk, reset, d;
4   output q;
5   reg q;
6
7   always @(posedge clk or negedge reset)
8     if(!reset) q <= 0;
9     else q <= d;
10
11 endmodule
```

List 2 shows an example of the test bench for flip flop. The frequency of *clk* is 10MHz (i.e. 100ns).

4 Counter

Let us design N-bit counter whose specification is defined in List 2 The counter has four 1-bit input *clk*, *reset*, *load*, and

List 2: Test bench for Flip flop ff.v

```

1 'timescale 1ns/1ps
2 module ff_tb;
3
4 reg clk,reset,d;
5 wire q;
6
7 ff ff0(.clk(clk),.reset(reset),.d(d),.q(q));
8
9 initial begin
10 clk = 0;
11 forever
12 #50 clk = ~clk;
13 end
14
15 initial begin
16 reset = 0; d = 0;
17 #100 reset = 1; d = 1;
18 #200 d = 0;
19 #200 d = 1;
20 #100 reset = 0;
21 #100 reset = 1;
22 #200 d = 1;
23 #100 d = 0;
24 end
25
26 endmodule

```

inc. It also has N-bit input d and N-bit output q.

Table 2: Specification of a counter

input				output
clk	reset	load	inc	q
-	0	-	-	0 (asynchronous reset)
↑	1	1	0	d (synchronous latch)
↑	1	0	1	q+1 (increment)
↑	1	0	0	q (keeps the same value)
not ↑	1	-	-	q (keeps the same value)

List 3 is a Verilog HDL description of an N-bit counter. The default value of N is 16.

List 5 is a UCF file for a counter. If you have an error, then add a new constraint `CLOCK_DEDICATED_ROUTE = FALSE;` to the `BTN_EAST` (i.e. `clk`).

5 State machine

Figure 1 illustrates the state machine for CPU that we will design later of this course. Two states `FETCHA` and `FETCHB`

List 3: N-bit Counter counter.v

```

1 module counter(clk,reset,load,inc,d,q);
2 parameter N = 16;
3
4 input clk,reset,load,inc;
5 input [N-1:0] d;
6 output [N-1:0] q;
7 reg [N-1:0] q;
8
9 always @(posedge clk or negedge reset)
10 if(!reset) q <= 0;
11 else if(load) q <= d;
12 else if(inc) q <= q + 1;
13
14 endmodule

```

List 4: Test bench for a counter counter_tb.v

```

1 'timescale 1ns / 1ps
2 module counter_tb;
3
4 reg clk,reset,load,inc;
5 reg [15:0] d;
6 wire [15:0] q;
7 counter counter0(.clk(clk), .reset(reset), .load(load), .inc(inc)
8 , .d(d), .q(q));
9
10 initial begin
11 clk = 0;
12 forever
13 #50 clk = ~clk;
14 end
15
16 initial begin
17 reset = 0; load = 0; inc = 0; d=16'h0000;
18 #100 reset = 1;
19 #100 inc = 1;
20 #300 inc = 0; load = 1; d = 16'h1234;
21 #100 inc = 1; load = 0; d = 16'h0000;
22 #500 reset = 0;
23 end
24 endmodule

```

List 5: top module counter_top.v

```

1 module counter_top(BTN_NORTH, BTN_EAST, BTN_WEST,
2 BTN_SOUTH, LED);
3 input BTN_NORTH, BTN_EAST, BTN_WEST,
4 BTN_SOUTH;
5 output [7:0] LED;
6
7 counter #(8) counter0(.clk(BTN_EAST),.reset(~
8 BTN_SOUTH),.load(BTN_NORTH),.inc(BTN_WEST),.
9 d(8'h55),.q(LED));
10 endmodule

```

List 6: UCF file for counter_top.ucf(Spartan-3A/3AN Starter kit)

```

1 # PUSH SWITCH
2 NET "BTN_NORTH" LOC = "T14" | IOSTANDARD =
  LVTTTL | PULLDOWN ;
3 NET "BTN_EAST" LOC = "T16" | IOSTANDARD = LVTTTL
  | PULLDOWN ;
4 NET "BTN_WEST" LOC = "U15" | IOSTANDARD = LVTTTL
  | PULLDOWN ;
5 NET "BTN_SOUTH" LOC = "T15" | IOSTANDARD =
  LVTTTL | PULLDOWN ;
6
7 # LED
8 NET "LED<7>" LOC = "W21" | IOSTANDARD = LVTTTL |
  SLEW = QUIETIO | DRIVE = 4 ;
9 NET "LED<6>" LOC = "Y22" | IOSTANDARD = LVTTTL |
  SLEW = QUIETIO | DRIVE = 4 ;
10 NET "LED<5>" LOC = "V20" | IOSTANDARD = LVTTTL |
  SLEW = QUIETIO | DRIVE = 4 ;
11 NET "LED<4>" LOC = "V19" | IOSTANDARD = LVTTTL |
  SLEW = QUIETIO | DRIVE = 4 ;
12 NET "LED<3>" LOC = "U19" | IOSTANDARD = LVTTTL |
  SLEW = QUIETIO | DRIVE = 4 ;
13 NET "LED<2>" LOC = "U20" | IOSTANDARD = LVTTTL |
  SLEW = QUIETIO | DRIVE = 4 ;
14 NET "LED<1>" LOC = "T19" | IOSTANDARD = LVTTTL |
  SLEW = QUIETIO | DRIVE = 4 ;
15 NET "LED<0>" LOC = "R20" | IOSTANDARD = LVTTTL |
  SLEW = QUIETIO | DRIVE = 4 ;

```

are used to fetch instruction codes from a memory, and EX-ECA and EXECB are used to execute an instruction according to the instruction code. Since the state machine has 5 states, three bits are used to store the current state.

List 7 is a state machine for CPU and List 8 is its test bench.

List 7: State machine state.v

```

1 'define IDLE 3'b000
2 'define FETCHA 3'b001
3 'define FETCHB 3'b010
4 'define EXECA 3'b011
5 'define EXECB 3'b100
6
7 module state(clk,reset,run,cont,halt,cs);
8
9   input clk, reset, run, cont, halt;
10  output [2:0] cs;
11  reg [2:0] cs;
12
13  always @(posedge clk or negedge reset)
14    if(!reset) cs <= 'IDLE;
15    else
16      case(cs)
17        'IDLE: if(run) cs <= 'FETCHA;
18        'FETCHA: cs <= 'FETCHB;
19        'FETCHB: cs <= 'EXECA;
20        'EXECA: if(halt) cs <= 'IDLE;
21                else if(cont) cs <= 'EXECB;
22                else cs <= 'FETCHA;
23        'EXECB: cs <= 'FETCHA;
24        default: cs <= 3'bxxx;
25      endcase
26
27 endmodule

```

6 Stack

Stack is a Last In First Out (LIFO) memory, which is used to store intermediate value for evaluating formula. Stack has 5 1-bit input clk, reset, load, push, pop, 16-bit input d, and 2 16-bit outputs qtop, qnext. Also, it has an array of 16-bit registers. 3 inputs load, push, pop are used to control the array of registers.

7 Operation Stack

An operation stack consists of stack and ALU. The operation stack is used to evaluate the postfix notation of formulas. For

 


Figure 1: State machine

 


Figure 2: Behavior of Stack

List 8: Test bench state_tb.v

```

1  'timescale 1ns / 1ps
2  module state_tb;
3
4      reg clk,reset,run,halt,cont;
5      wire [2:0] cs;
6
7      state state0(.clk(clk),.reset(reset),.run(run),.cont(cont),.halt(
8          halt),.cs(cs));
9
10     initial begin
11         clk = 0;
12         forever
13             #50 clk = ~clk;
14     end
15
16     initial begin
17         reset = 0; run = 0; halt = 0; cont = 0;
18         #100 reset = 1; run = 1;
19         #100 run = 0;
20         #200 cont = 1;
21         #100 cont = 0;
22         #600 halt = 1;
23         #100 halt = 0;
24     end
25 endmodule

```

List 9: Top module state_top.v of the state machine

```

1  'define IDLE 3'b000
2  'define FETCHA 3'b001
3  'define FETCHB 3'b010
4  'define EXECA 3'b011
5  'define EXECB 3'b100
6
7  module state_top(BTN_EAST, BTN_SOUTH, SW, LED);
8      input BTN_EAST, BTN_SOUTH;
9      input [2:0] SW;
10     output [4:0] LED;
11     wire [2:0] cs;
12
13     state state0(.clk(BTN_EAST),.reset(~BTN_SOUTH),.run(
14         SW[2]),.cont(SW[1]),.halt(SW[0]),.cs(cs));
15
16     assign LED[4] = (cs == 'IDLE);
17     assign LED[3] = (cs == 'FETCHA);
18     assign LED[2] = (cs == 'FETCHB);
19     assign LED[1] = (cs == 'EXECA);
20     assign LED[0] = (cs == 'EXECB);
21 endmodule

```

List 10: UCF state_top.ucf for state machine(Spartan-3A/3AN)

```

1  # PUSH SWITCH
2  NET "BTN_EAST" LOC = "T16" | IOSTANDARD = LVTTTL
3  | PULLDOWN ;
4  NET "BTN_SOUTH" LOC = "T15" | IOSTANDARD =
5  LVTTTL | PULLDOWN ;
6
7  # LED
8  NET "LED<4>" LOC = "V19" | IOSTANDARD = LVTTTL |
9  SLEW = QUIETIO | DRIVE = 4 ;
10 NET "LED<3>" LOC = "U19" | IOSTANDARD = LVTTTL |
11 SLEW = QUIETIO | DRIVE = 4 ;
12 NET "LED<2>" LOC = "U20" | IOSTANDARD = LVTTTL |
13 SLEW = QUIETIO | DRIVE = 4 ;
14 NET "LED<1>" LOC = "T19" | IOSTANDARD = LVTTTL |
15 SLEW = QUIETIO | DRIVE = 4 ;
16 NET "LED<0>" LOC = "R20" | IOSTANDARD = LVTTTL |
17 SLEW = QUIETIO | DRIVE = 4 ;
18
19 # SLIDE SWITCH
20 NET "SW<2>" LOC = "U8" | IOSTANDARD = LVTTTL |
21 PULLUP ;
22 NET "SW<1>" LOC = "U10" | IOSTANDARD = LVTTTL |
23 PULLUP ;
24 NET "SW<0>" LOC = "V8" | IOSTANDARD = LVTTTL |
25 PULLUP ;

```

example, usual formula uses infix notation as follows:

$$(1 + 2) * (3 + 4)$$

To evaluate this formula on the operation stack, the postfix notation below are used:

$$1 \ 2 \ + \ 3 \ 4 \ + \ *$$

Table 3 shows the specification of the operation stack.

List 12 shows an Verilog HDL description of operation stack. It instantiates ALU and stack.

List 13 is an example of a test bench for operation stack. In this example, the infix notation of the following formula is evaluated.

$$(-(2 + 3 * 4) < 5) || (6 > 7)$$

This infix notation must be converted to the postfix notation as follows:

$$2 \ 3 \ 4 \ * \ + \ - \ 5 \ < \ 6 \ 7 \ > \ ||$$

8 Homework

Homework 1 Design 4-bit counter by instantiating 4 flip flops and 4 full adders. The 4 flip flops are used to store

Table 3: Operation Stack

input				operation	load	push	behavior	
clk	reset	num	op				pop	d
-	0	-	-	asynchronous reset	-	-	-	-
↑	1	1	-	push x	1	1	0	x
↑	1	-	1	operation specified by x	1	0	1 (binary operation) 0 (unary operation)	s of alu

List 11: Stack stack.v

```

1 module stack(clk, reset, load, push, pop, d, qtop, qnext);
2
3   input clk, reset, load, push, pop;
4   input [15:0] d;
5   output [15:0] qtop, qnext;
6   reg [15:0] q [3:0];
7
8   assign qtop = q[0];
9   assign qnext = q[1];
10
11  always @(posedge clk or negedge reset)
12    if(!reset) q[0] <= 0;
13    else if(load) q[0] <= d;
14    else if(pop) q[0] <= q[1];
15
16  always @(posedge clk or negedge reset)
17    if(!reset) q[1] <= 0;
18    else if(push) q[1] <= q[0];
19    else if(pop) q[1] <= q[2];
20
21  always @(posedge clk or negedge reset)
22    if(!reset) q[2] <= 0;
23    else if(push) q[2] <= q[1];
24    else if(pop) q[2] <= q[3];
25
26  always @(posedge clk or negedge reset)
27    if(!reset) q[3] <= 0;
28    else if(push) q[3] <= q[2];
29
30 endmodule

```

List 12: Operation stack opstack.v

```

1 module opstack(clk,reset,num,op,x);
2
3   input clk, reset, num, op;
4   input [15:0] x;
5   wire [15:0] qtop, qnext, aluout;
6   wire load, push, pop;
7   reg [15:0] stackin;
8
9   alu alu0(.a(qtop), .b(qnext), .f(x[4:0]), .s(aluout));
10  stack stack0(.clk(clk), .reset(reset), .load(load), .push(push),
11             .pop(pop), .d(stackin), .qtop(qtop), .qnext(qnext));
12
13  assign load = num | op;
14  assign push = num;
15  assign pop = op & ~x[4];
16
17  always @(num or op or x or aluout)
18    if(num) stackin = x;
19    else if(op) stackin = aluout;
20    else stackin = 16'hxxxx;
21 endmodule

```

List 13: Test bench opstack_tb.v for operation stack

```

1  `timescale 1ns / 1ps
2
3  `define ADD 5'b00000
4  `define SUB 5'b00001
5  `define MUL 5'b00010
6  `define SHL 5'b00011
7  `define SHR 5'b00100
8  `define BAND 5'b00101
9  `define BOR 5'b00110
10 `define BXOR 5'b00111
11 `define AND 5'b01000
12 `define OR 5'b01001
13 `define EQ 5'b01010
14 `define NE 5'b01011
15 `define GE 5'b01100
16 `define LE 5'b01101
17 `define GT 5'b01110
18 `define LT 5'b01111
19 `define NEG 5'b10000
20 `define BNOT 5'b10001
21 `define NOT 5'b10010
22
23 module opstack_tb;
24
25     reg clk, reset, num, op;
26     reg [15:0] x;
27
28     opstack opstack0(.clk(clk), .reset(reset), .num(num), .op(op)
29         , .x(x));
30
31     initial begin
32         clk = 0;
33         forever
34             #50 clk = ~clk;
35     end
36
37     initial begin
38         reset = 0; num = 0; op = 0; x = 0;
39         #100 reset = 1; num = 1; op = 0; x = 2;
40         #100 num = 1; op = 0; x = 3;
41         #100 num = 1; op = 0; x = 4;
42         #100 num = 0; op = 1; x = 'MUL;
43         #100 num = 0; op = 1; x = 'ADD;
44         #100 num = 0; op = 1; x = 'NEG;
45         #100 num = 1; op = 0; x = 5;
46         #100 num = 0; op = 1; x = 'LT;
47         #100 num = 1; op = 0; x = 6;
48         #100 num = 1; op = 0; x = 7;
49         #100 num = 0; op = 1; x = 'GT;
50         #100 num = 0; op = 1; x = 'OR;
51         #100 num = 0; op = 0; x = 0;
52     end
53 endmodule

```

4-bit integer, and the 4 full adders are used to compute plus one (+1). Write the test bench for it and perform the simulation to confirm that it works properly. Also you need to write the illustration of the diagram of this 4-bit counter.

Homework 2 Design a state machine with 6 states as follows:

- 6 states are assigned using 3 bits as follows: State0: 3'b000, State1: 3'b001, State2: 3'b010, State3: 3'b011, State4: 3'b100, State5: 3'b101.
- 2 control inputs nextstate and jumpstate are used as follows: If the current state is State i and nextstate is 1, then next state is State (i+1 mod 6). If the current state is State i and jumpstate is 1, then next state is State (i+2 mod 6). If both control bits are 0, then the state is not changed.

Homework 3 Extend the stack (List 11) such that it has six 16-bit registers. After that, write the infix notation of a formula that has at least 10 operations. Convert it to the postfix notation, and write the test bench to evaluate the formula on the operation stack. Perform the simulation.